
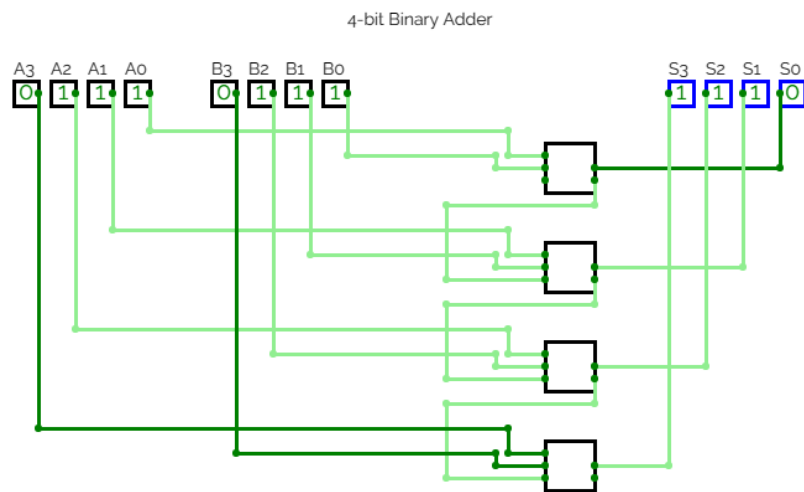


Assignment-8
Sambhav Kaushik | SK10 | 22220CMP023

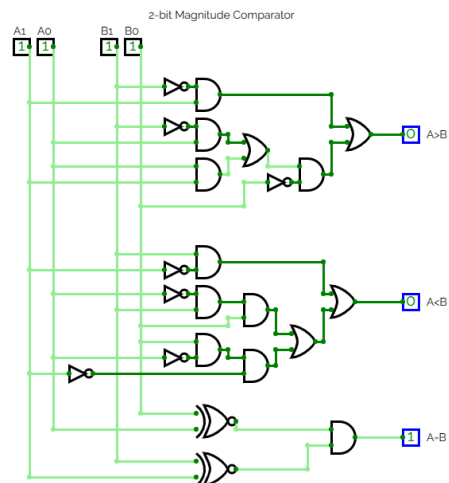
- **Problem 1:** 4-bit Binary parallel Adder.



- **problem 2:** 2 bit Magnitude Comparator.



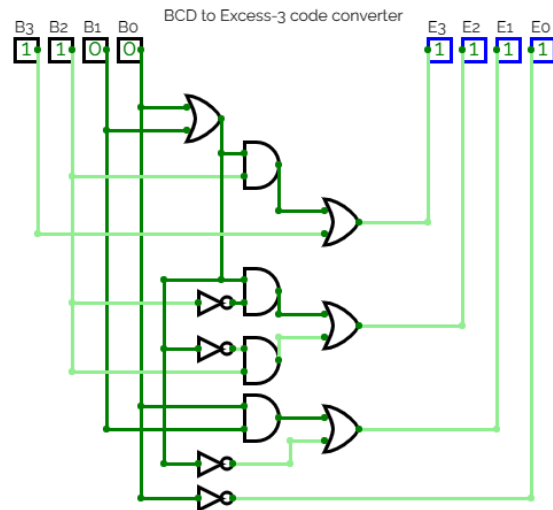- **problem 3:** Design a BCD to Excess-3 code converter.



- **problem 4:** Design a Binary to Gray Code Converter.

