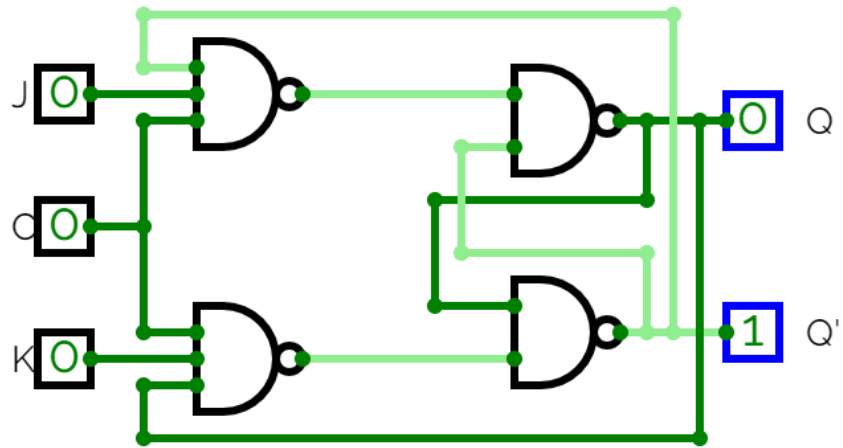


**Assignment-11**  
**Sambhav Kaushik | SK10 | 22220CMP023**


- **Problem 1:** Design JK flip flop using NAND gate.

Design JK flip flop using NAND gate




- **Problem 2:** Design T flip flop using NAND gates.

Design T flip flop using NAND gates

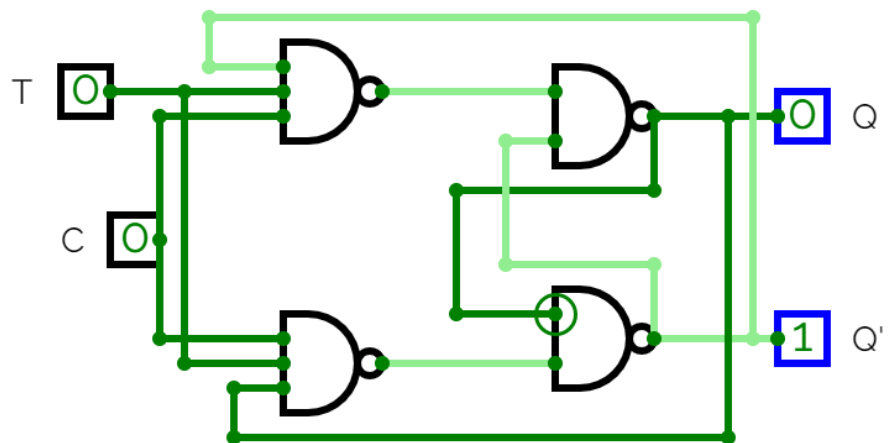

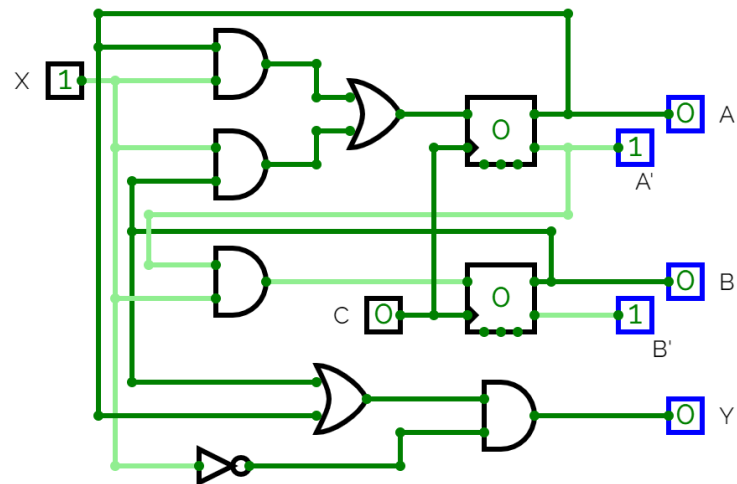- **problem 3:** Consider the sequential circuit using D flip flop discussed in the class. Analyse the circuit behaviour for the given inputs.

Consider the sequential circuit using D flip flop discussed in the class




**State Table:**

Present cell		Next state		Output (Y)	
A	B	AB (X=0)	AB (X=1)	X=0	X=1
0	0	00	01	0	0
0	1	00	11	1	0
1	0	00	10	1	0
1	1	00	10	1	0

**State Functions:**

1.  $A(t+1) = A(t).X(t) + B(t).X(t)$
2.  $B(t+1) = A'(t).X(t)$
3.  $Y(t) = X'.(A(t) + B(t))$

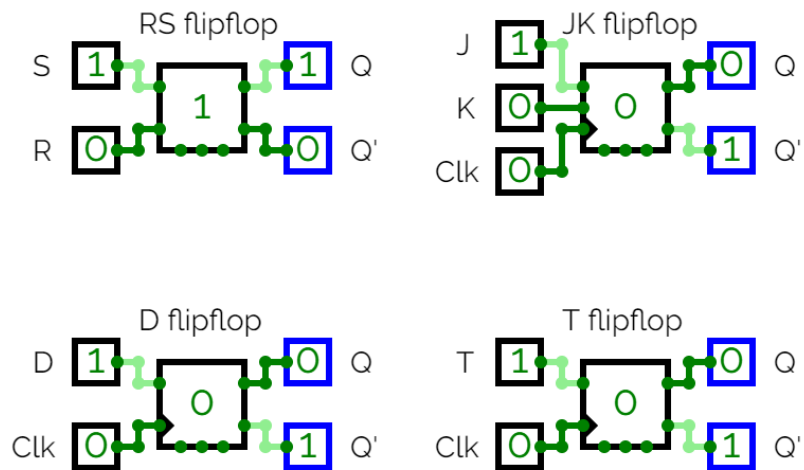- **problem 4:** Verify the circuit excitation table for:
  - i. RS flipflop
  - ii J-K flipflop
  - iii. D flipflop
  - iv. T flipflop



**SR flipflop Excitation Table:**

Q(n)	Q(n+1)	S	R
0	0	0	X
1	0	X	1
0	1	1	X
1	1	X	0

**JK flipflop Excitation Table:**

Q(n)	Q(n+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**D flipflop Excitation Table:**

Q(n)	Q(n+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

**T flipflop Excitation Table:**

Q(n)	Q(n+1)	T
0	0	0
0	1	1
1	0	1
1	1	0