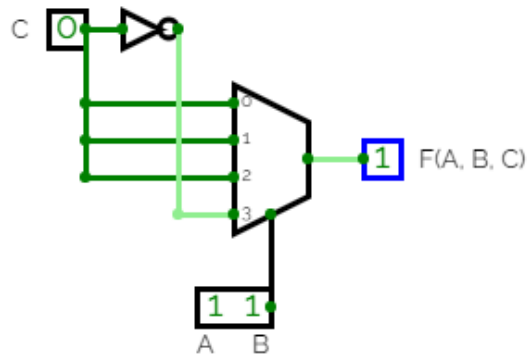


Assignment-9
Sambhav Kaushik | SK10 | 22220CMP023


- **Problem 1:** Implement Boolean function $F(A, B, C) = \Sigma(1, 3, 5, 6)$ using MUX.

Implement Boolean function $F(A, B, C) = \Sigma(1, 3, 5, 6)$ using MUX




- **Problem 2:** Implement Full-Adder using Decoder.

Implement Full-Adder using Decoder

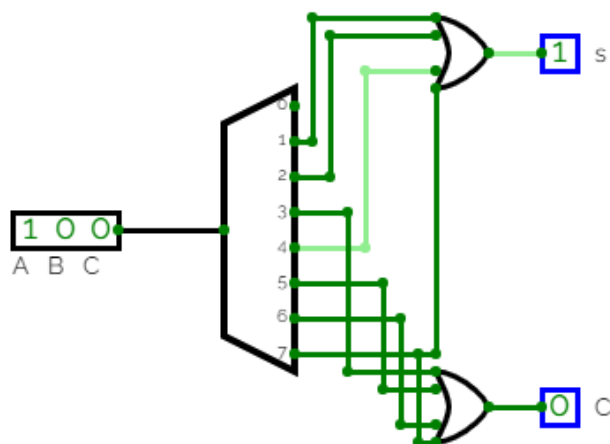

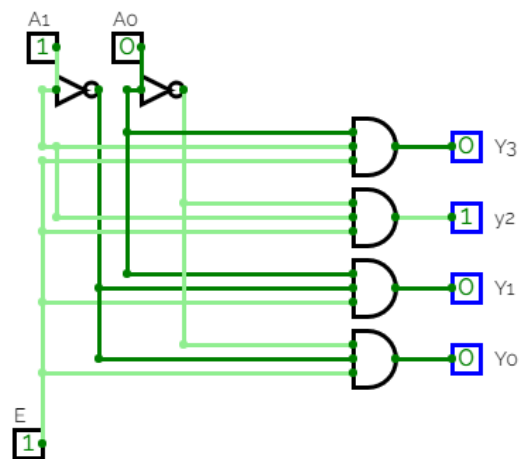- **problem 3:** Design a 2 to 4 line Decoder with Enable input.

Design a 2 to 4 line Decoder with Enable input



- **problem 4:** Design a 1:4 line Demux.

Design a 1:4 line De-MUX

