 



**Assignment-10**  
**Sambhav Kaushik | SK10 | 22220CMP023**

- **Problem 1:** Design a SR latch using NAND gates.



S	R	Q(n)	Q(n+1)
0	0	0	INVALID
0	0	1	INVALID
0	1	0	1 (Reset)
0	1	1	1 (Reset)
1	0	0	0 (Set)
1	0	1	0 (Set)
1	1	0	0 (Memory)
1	1	1	1 (Memory)

 
- **Problem 2:** Design SR latch using NOR gates.



S	R	Q(n)	Q(n+1)
0	0	0	0 (Memory)
0	0	1	1 (Memory)
0	1	0	0 (Reset)
0	1	1	0 (Reset)
1	0	0	1 (Set)
1	0	1	1 (Set)
1	1	0	INVALID
1	1	1	INVALID

 - **problem 3:** Design SR latch with control input using NAND gates.


SR latch with control input using NAND gates



Clog	S	R	Q(n)	Q(n+1)
Untriggered	X	X	0	0 (Memory)
Untriggered	X	X	1	1 (Memory)
Triggered	0	0	0	0 (Memory)
Triggered	0	0	1	1 (Memory)
Triggered	0	1	0	0 (Reset)
Triggered	0	1	1	0 (Reset)
Triggered	1	0	0	1 (Set)
Triggered	1	0	1	1 (Set)
Triggered	1	1	0	INVALID
Triggered	1	1	1	INVALID

- **problem 4:** Design D flip flop using NAND gate.

### D flip flop using NAND gate

 

Clock	D	Q(n)	Q(n+1)
Untriggered	X	0	0
Untriggered	X	1	1
Triggered	0	0	0
Triggered	0	1	0
Triggered	1	0	1
Triggered	1	1	1